

# KATHMANDU UNIVERSITY

SCHOOL OF ENGINEERING

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

## LAB REPORT 06



**EEEG-321**

Department of Electrical and Electronics Engineering

**By:**

Samyam Shrestha (32056)

**To:**

Santosh Shaha Sir

**Date:**

**4<sup>th</sup> June, 2024**

# Title: Write VHDL D and T flipflop

Requirements: Vivado Software, Laptop, FPGA board

## 1) D flipflop

### VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity d_flipflop_56 is
port (
din : in std_logic;
clk: in std_logic;
rst: in std_logic;
q: out std_logic);
end d_flipflop_56;

architecture Behavioral of d_flipflop_56 is
begin
dff: process (clk, rst, din) begin
if (rst = '1') then
q <= '0';
elsif (clk' event and clk = '1') then
q <= din;
end if;
end process dff;
end Behavioral;
```

### Test Bench code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity dflipflop_tb_56 is
end dflipflop_tb_56;

architecture Behavioral of dflipflop_tb_56 is
component d_flipflop_56
port (
din : in std_logic;
clk: in std_logic;
rst: in std_logic;
q: out std_logic);
end component;

signal din: std_logic;
signal clk: std_logic;
signal rst: std_logic;
```

```

signal q: std_logic;

begin
  uut: d_flipflop_56 port map ( din => din,
    clk => clk,
    rst => rst,
    q => q);
  stimulus: process begin
    clk <= '0';
    wait for 10ns;
    clk <= '1';
    wait for 10ns;
  end process;
  stimuli: process begin
    din <= '0';
    wait for 10ns;
    din <= '1';
    wait for 10ns;
  end process;
  stimuls: process begin
    rst <= '0';
    wait for 100ns;
    rst <= '1';
    wait for 10ns;
  end process;
end Behavioral;

```

### RTL Schematic Diagram:

 


Figure 1: RTL Schematic of D flip-flop

Simulation Model:

The simulation results are depicted in the figure below, showcasing the D flip-flop output values.

 


Figure 2: Simulation Model of D flip-flop

XDC File

```
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports din]
set_property IOSTANDARD LVCMOS33 [get_ports q]
set_property IOSTANDARD LVCMOS33 [get_ports rst]
```

Device Utilization Report:

 


Figure 3: Device Utilization Report

Timing Analysis Report:

Design Timing Summary					
Setup		Hold		Pulse Width	
Worst Negative Slack (WNS): inf		Worst Hold Slack (WHS): inf		Worst Pulse Width Slack (WPWS): NA	
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns		Total Pulse Width Negative Slack (TPWS): NA	
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0		Number of Failing Endpoints: NA	
Total Number of Endpoints: 3		Total Number of Endpoints: 3		Total Number of Endpoints: NA	
There are no user specified timing constraints.					

Figure 4: Timing Summary

## 2) T flip-flop

### VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity t_56 is
port (
tin: in std_logic;
clk: in std_logic;
rst: in std_logic;
q: out std_logic);
end t_56;

architecture Behavioral of t_56 is
begin
tff: process (clk, rst, tin) is
variable m: std_logic := '0';
begin
if (rst = '1') then
m := '0';
elsif (rising_edge(clk)) then
if (tin = '1') then
m := not m;
end if;
end if;
q <= m;
end process tff;
end Behavioral;
```

### Test Bench Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity t_tb is
end t_tb;

architecture Behavioral of t_tb is
component t_56
port (
tin: in std_logic;
clk: in std_logic;
rst: in std_logic;
q: out std_logic);
end component;
```

```
signal tin: std_logic;
signal clk: std_logic;
signal rst: std_logic;
signal q: std_logic;
signal m: std_logic;
begin
    uut : t_56 port map ( tin => tin,
        clk => clk,
        rst => rst,
        q => q);
```

```
stimulus: process begin
    clk <= '0';
    wait for 10ns;
    clk <= '1';
    wait for 10ns;
end process;
```

```
stimuli: process begin
    tin <= '0';
    wait for 10ns;
    tin <= '1';
    wait for 100ns;
end process;
stim: process begin
    rst <= '0';
    wait for 100ns;
    rst <= '1';
    wait for 10ns;
end process;
stt: process begin
    m <= '0';
    wait for 10ns;
    m <= '1';
    wait for 100ns;
end process;
end Behavioral;
```

## RTL Schematic

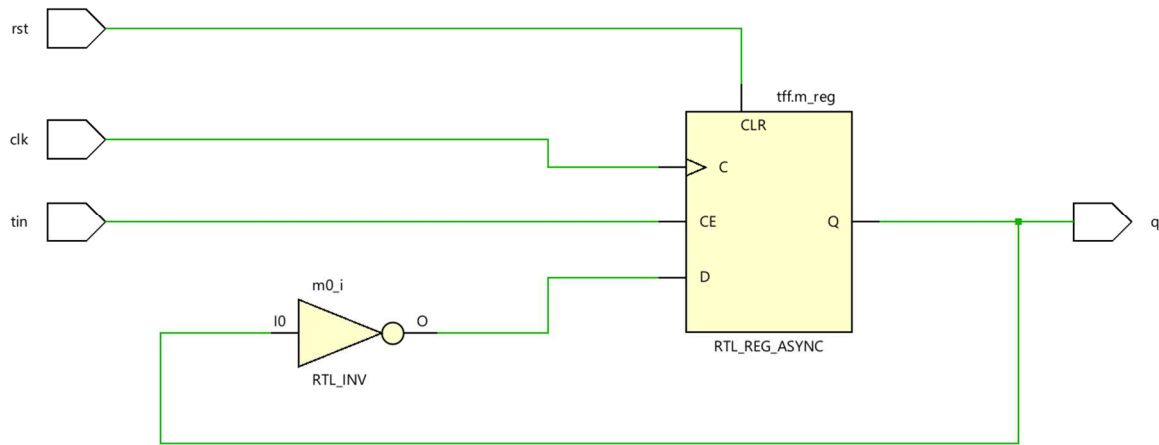


Figure 5: RTL Schematic of T flip-flop

## XDC File

```
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports q]
set_property IOSTANDARD LVCMOS33 [get_ports rst]
set_property IOSTANDARD LVCMOS33 [get_ports tin]
```

## Simulation

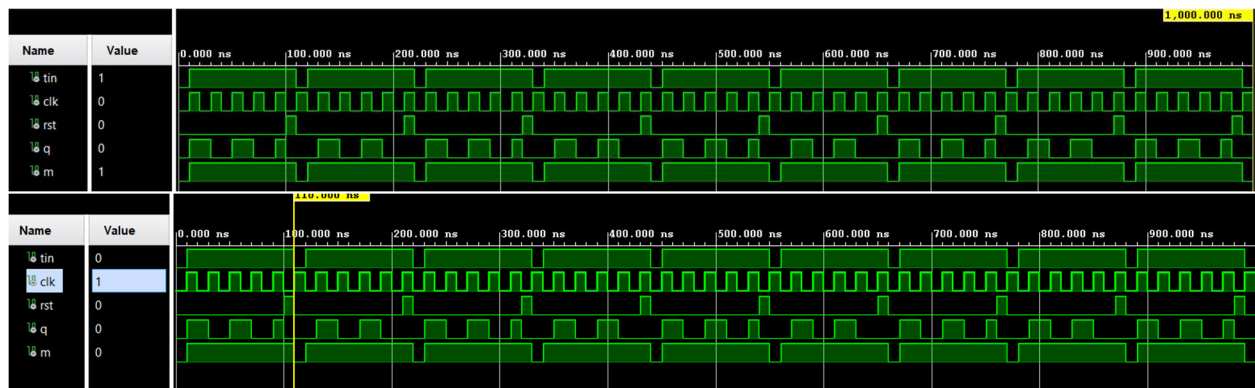


Figure 6: Timing Diagram for T flip-flop

## Device Utilization Report

### Summary

Resource	Utilization	Available	Utilization %
LUT	1	32600	0.00
FF	1	65200	0.00
IO	4	210	1.90

 


Figure 7: Device Utilization Report

## Time Analysis Report

### Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 3	Total Number of Endpoints: 3	Total Number of Endpoints: NA

There are no user specified timing constraints.

Figure 8: Timing Summary for Full Adder

## Conclusion

In summary, we developed and tested VHDL code for a D and T flip-flop using Vivado. Additionally, troubleshooting steps were provided to resolve potential file access errors during simulation, such as ensuring no other processes are using the log file, manually deleting the file, and cleaning and rebuilding the project in Vivado. This comprehensive approach ensures that the counter operates correctly and that any issues encountered during simulation are addressed effectively.