

KATHMANDU UNIVERSITY

SCHOOL OF ENGINEERING

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

LAB REPORT 01



EEEG-321

Department of Electrical and Electronics Engineering

By:

Samyam Shrestha (31056)

To:

Santosh Shah Sir

Date:

9th April, 2024

Title: Implement Half Adder / Full Adder / Subtraction using VHDL

Requirements: Vivado Software, Laptop

1) Half Adder

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity lab01_56 is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          S : out STD_LOGIC;
          C : out STD_LOGIC);
end lab01_56;

architecture Behavioral of lab01_56 is
begin
    S <= A XOR B;
    C <= A AND B;
end Behavioral;
```

Test Bench code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Lab1_56_tb is
-- Port ( );
end Lab1_56_tb;

architecture Behavioral of Lab1_56_tb is
    component lab01_56
        Port(a: IN std_logic;
             b: IN std_logic;
             c: OUT std_logic;
             s: OUT std_logic);
    end component;

    signal A: std_logic : = '0';
    signal B: std_logic : = '0';
    signal C: std_logic : = '0';
    signal S: std_logic : = '0';

begin

    UUT lab01_56 Port Map (
        A => a;
        B => b;
        S => s;
```

$C \Rightarrow c$;

```
stimuli : process begin
    wait for 10ns;
    A <= '0';
    B <= '0';
    wait for 10ns;
    A <= '0';
    B <= '1';
    wait for 10ns;
    A <= '1';
    B <= '0';
    wait for 10ns;
    A <= '1';
    B <= '1';
    wait;
end process;
end Behavioral;
```

RTL Schematic Diagram:

 


Figure 1: RTL Schematic Diagram

Simulation Model:

Here, A and B are two input signals. S = Sum and C = Carry. The generated waveform for different combinations for input is shown in the figures below.

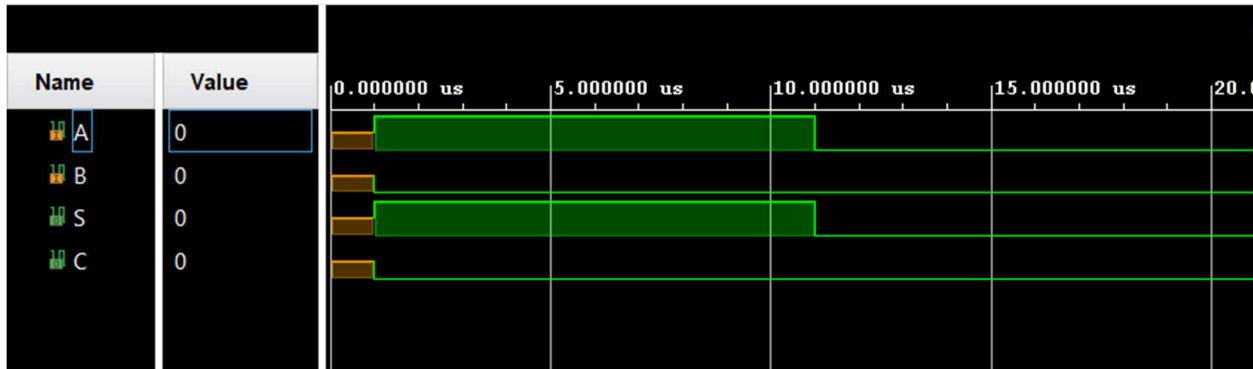


Figure 2: A=0, B=0 S=0, C=0

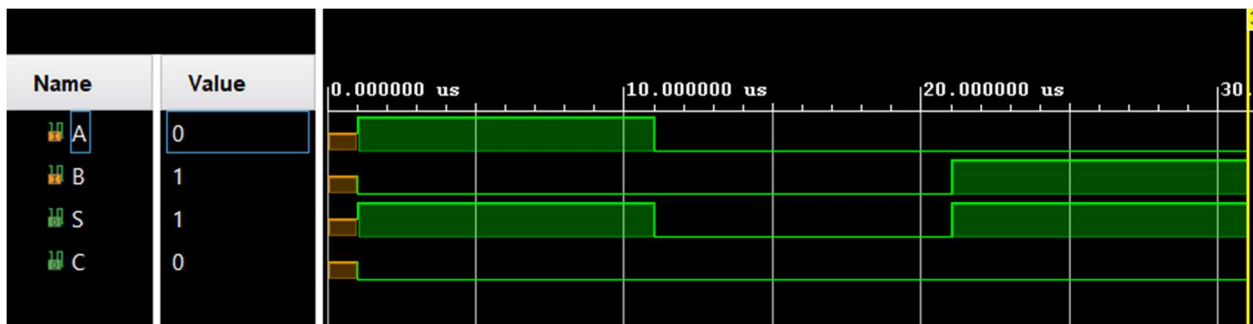


Figure 3: A=0, B=1, S=1, C= 0

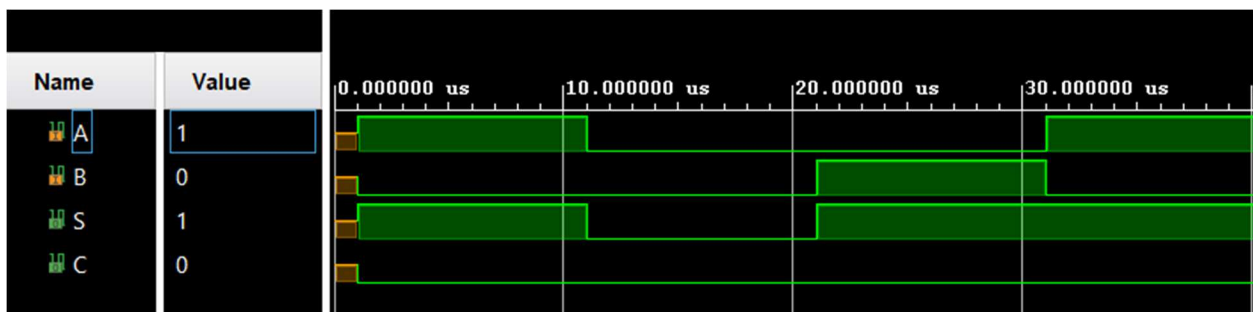


Figure 4: A=1, B= 0, S=1, C=0

 


Figure 5: A=1, B=1, S=0, C=1

Device Utilization Report:

 


Figure 6: Device Utilization Report

Timing Analysis Report:

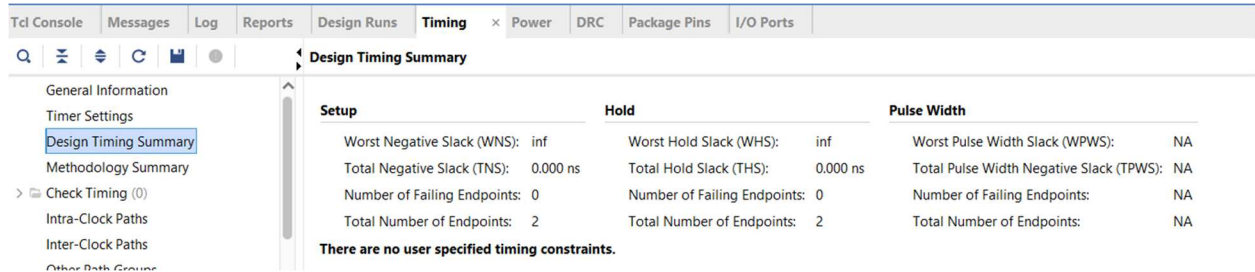


Figure 7: Timing Summary for Half Adder

2) Full Adder

VHDL Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fulladder_56 is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : in STD_LOGIC;
          Carry : out STD_LOGIC;
          Sum : out STD_LOGIC);
end fulladder_56;
```

architecture Behavioral of fulladder_56 is

```
begin  
Sum <= A XOR (B XOR C);  
Carry <= (A and B) OR (B and C) OR (A and C);  
end Behavioral;
```

Test Bench Code

```
library IEEE;  
use IEEE.Std_logic_1164.all;  
use IEEE.Numeric_Std.all;  
entity fulladder_56_tb is  
end;
```

architecture bench of fulladder_56_tb is

```
component fulladder_56  
  Port ( A : in STD_LOGIC;  
        B : in STD_LOGIC;  
        C : in STD_LOGIC;  
        Carry : out STD_LOGIC;  
        Sum : out STD_LOGIC);  
end component;
```

```
signal A: STD_LOGIC;  
signal B: STD_LOGIC;  
signal C: STD_LOGIC;  
signal Carry: STD_LOGIC;  
signal Sum: STD_LOGIC;
```

begin

```
uut: fulladder_56 port map ( A    => A,  
                           B    => B,  
                           C    => C,  
                           Carry => Carry,  
                           Sum   => Sum );
```

stimulus: process

```
begin  
a <= '0';  
b <= '0';  
c <= '0';  
wait for 10ns;  
a <= '0';  
b <= '0';  
c <= '1';
```

```

wait for 10ns;
a<= '0';
b <= '1';
c<= '0';
wait for 10ns;
a<= '0';
b <= '0';
c<= '1';
wait for 10ns;
a<= '1';
b <= '0';
c<= '1';
wait for 10ns;
a<= '1';
b <= '1';
c<= '0';
wait for 10ns;
a<= '1';
b <= '1';
c<= '1';
wait for 10ns;
wait;
end process;
end;

```

RTL Schematic

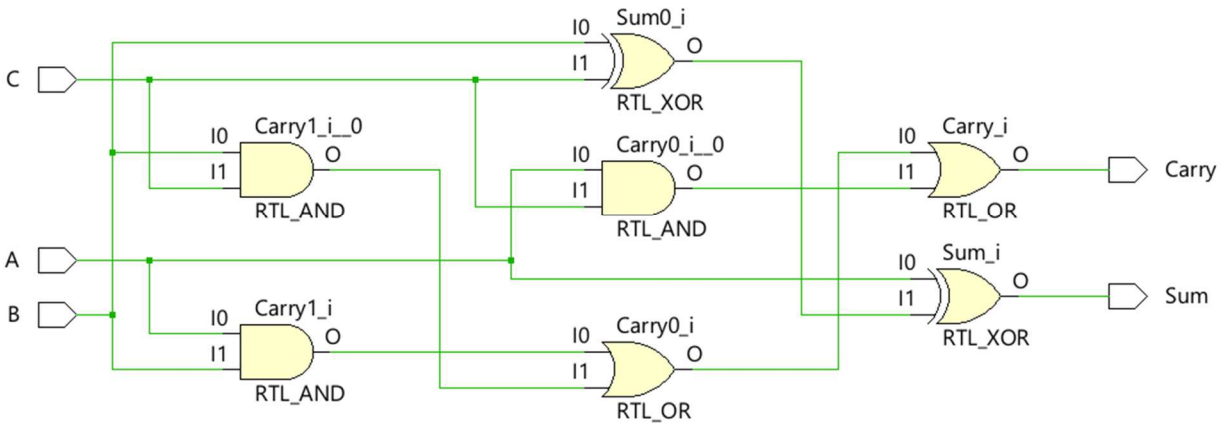


Figure 8: RTL Schematic of Full Adder

Simulation

The timing waveform graph for different possible combinations of input is given in the figure below. In a test-bench code, the different input combination was given and also the wait instruction for 10ns. So, while simulating, all the output can be seen in a single figure.

 


Figure 9: Timing Diagram for all the possible input combinations for full adder

Device Utilization Report

 


Figure 10: Device Utilization Report

Time Analysis Report

Design Timing Summary

| Setup | Hold | Pulse Width |
|--------------------------------------|----------------------------------|---|
| Worst Negative Slack (WNS): inf | Worst Hold Slack (WHS): inf | Worst Pulse Width Slack (WPWS): NA |
| Total Negative Slack (TNS): 0.000 ns | Total Hold Slack (THS): 0.000 ns | Total Pulse Width Negative Slack (TPWS): NA |
| Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 | Number of Failing Endpoints: NA |
| Total Number of Endpoints: 2 | Total Number of Endpoints: 2 | Total Number of Endpoints: NA |

There are no user specified timing constraints.

Figure 11: Timing Summary for Full Adder

3) Half Subtractor

VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity halfsubtractor_56 is
```



```

    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Diff : out STD_LOGIC;
          Borrow : out STD_LOGIC);
end halfsubtractor_56;

architecture Behavioral of halfsubtractor_56 is

begin
    Diff <= A XOR B;
    Borrow <= (NOT A) AND B;
end Behavioral;

```

Test-bench Code:

```

library IEEE;
use IEEE.Std_logic_1164.all;
use IEEE.Numeric_Std.all;

entity halfsubtractor_56_tb is
end;

architecture bench of halfsubtractor_56_tb is

    component halfsubtractor_56
        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              Diff : out STD_LOGIC;
              Borrow : out STD_LOGIC);
    end component;

    signal A: STD_LOGIC;
    signal B: STD_LOGIC;
    signal Diff: STD_LOGIC;
    signal Borrow: STD_LOGIC;

begin
    uut: halfsubtractor_56 port map ( A    => A,
                                     B    => B,
                                     Diff  => Diff,
                                     Borrow => Borrow );

    stimulus: process
    begin
        a<= '0';
        b<= '0';
        wait for 10ns;
        a<= '0';
        b<= '0';
        wait for 10ns;
        a<= '0';
    end process;

```

```

b<= '0';
wait for 10ns;
a<= '0';
b<= '0';
wait for 10ns;
wait;
end process;
end;

```

Simulation Model

Here in the waveform, for the input signal A and B = 0, the difference and borrow is also 0.

 


Figure 12: Simulation Diagram for Half Subtractor

RTL Schematic

 


Figure 13: RTL Schematic for Half Subtractor

Device Utilization Report

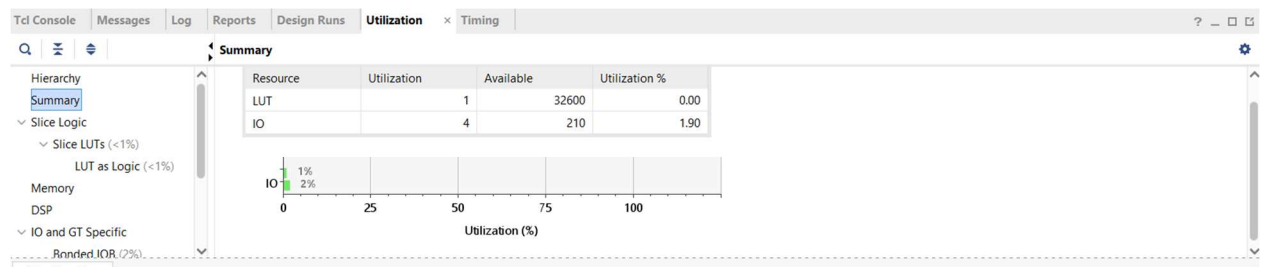


Figure 14: Utilization Report for Half Subtractor

Time Analysis Report

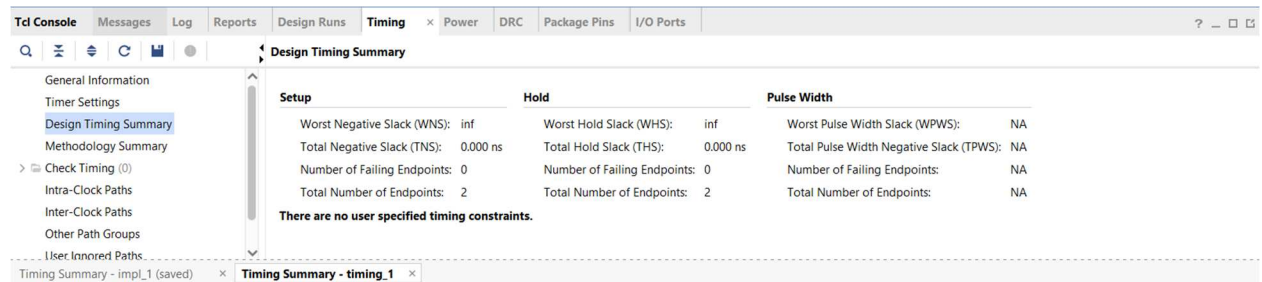


Figure 15: Timing Summary for Half Subtractor